

時序電路設計及應用


Homework 3

姓名：王品然

學號：113063572

Consider a design process for a duty-cycle corrector for a 1GHz input clock signal, denoted as clk_in . The output clock signal is denoted as clk_dcc . Once locked, clk_dcc will have a duty cycle very close to 50%.

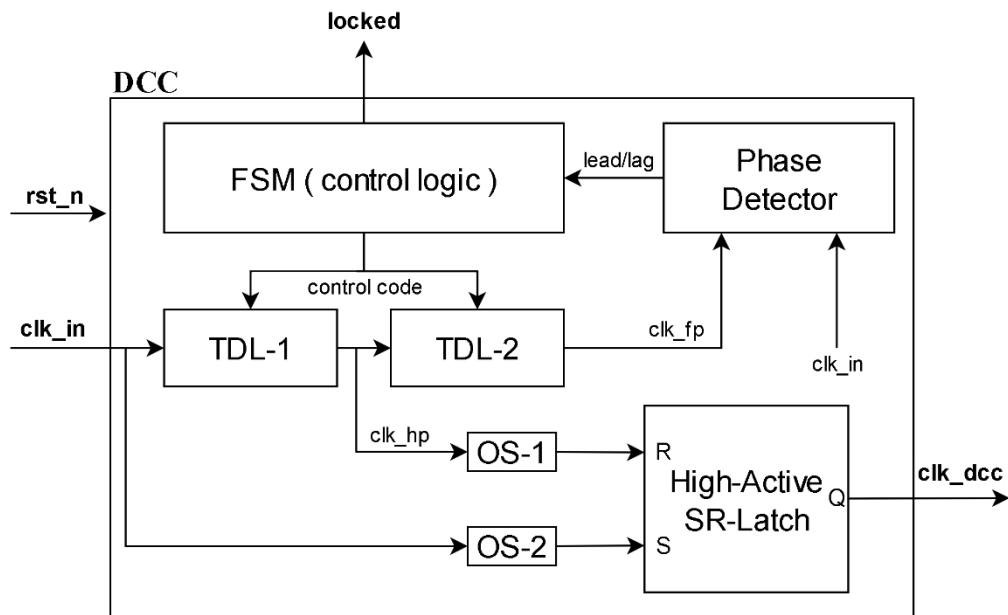- (a) (20%) Draw a **block diagram** of your design and summarizing how you plan to achieve the duty-cycle correction with a paragraph.




使用如上所示的 block diagram 可以實現 duty cycle 的修正，上半部的電路架構如同 Delay Locked Loop (DLL)， clk_in 訊號會經過兩個相同的 Tunable Delay Line (TDL)，且兩 TDL 由相同的 control code 所控制，從第二個 TDL 輸出的訊號(clk_fp)與 clk_in 當作 Phase Detector (PD)的輸入訊號，PD 會比較出現在 clk_fp 的 phase 是領先的或是落後的，並輸出 lead/lag 訊號做為指示 controller 做出 control code 改變的依據，在這個疊代的過程中， clk_in 和 clk_fp 的 phase error 會越來越小，直到 controller 鎖定 control code 確定 clk_fp 是 clk_in 延遲一個 cycle 的訊號。這裡需要特別注意一般的 DLL 可以鎖定在 clk_fp 為 clk_in 的整數倍周期的延遲，但這邊一定要是鎖定在一個週期，原因是要讓 clk_hp 剛好延遲半個週期。在 controller 做到以上工作後，讓 clk_in 與 clk_hp 分別經過一個 one shot circuit，以避免 clk_in 的 duty cycle 過大造成輸入 active high SR-latch 時，出現兩個輸入都為 1 的不合理情況。如此一來在最後一級的 SR-latch 會出現規律的 $(S,R)=(1,0)$ 和 $(S,R)=(0,1)$ ，每隔半周期交替出現，並在剩餘期間維持 $(S,R)=(0,0)$ ，也就是說每半周期 output(Q)會 toggle 一次並維持訊號直到下次 toggle，如此就完成了 duty cycle correction 的任務了。


- (b) (40%) **Realize the design as a synthesizable Verilog code.** (Your design can be a mixed format containing both netlists and RTL codes). (Hint: you may need Tunable Delay Lines, A Phase Detector, and a Controller, etc.) In this homework, we only need to use simple TDLs, e.g., path-selection-based TDLs, and some cell-based Phase Detector). Estimate your time resolution.

將(a)的 block diagram 中的子電路一一實現，以下展示電路圖或其架構，最後再附上 code：


(1) High-Active SR-Latch

 

(2) One Shot Based Oscillator

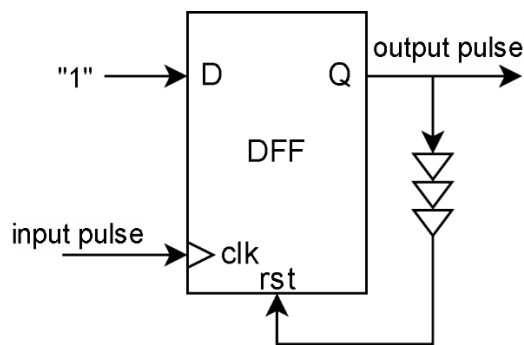


(3) Phase Detector

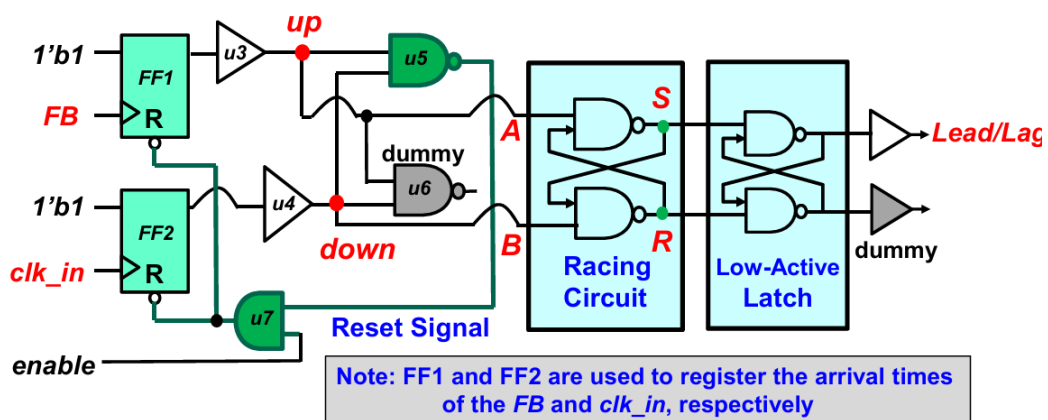

此電路圖截自講義


(4) Tunable Delay Line

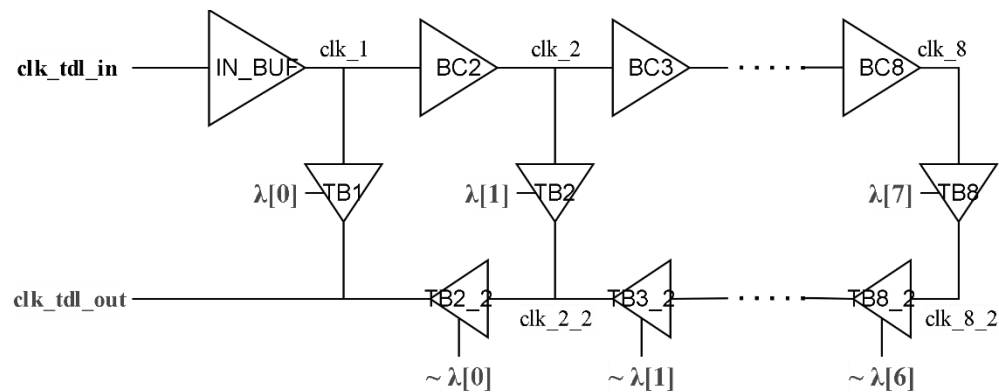

最終規格如下：IN_BUF 是 4 個 X1 的 CLKBUF 的 buffer chain；BC 是 2 個 X1 的 CLKBUF 的 buffer chain；TB 是一個 TBUF4。

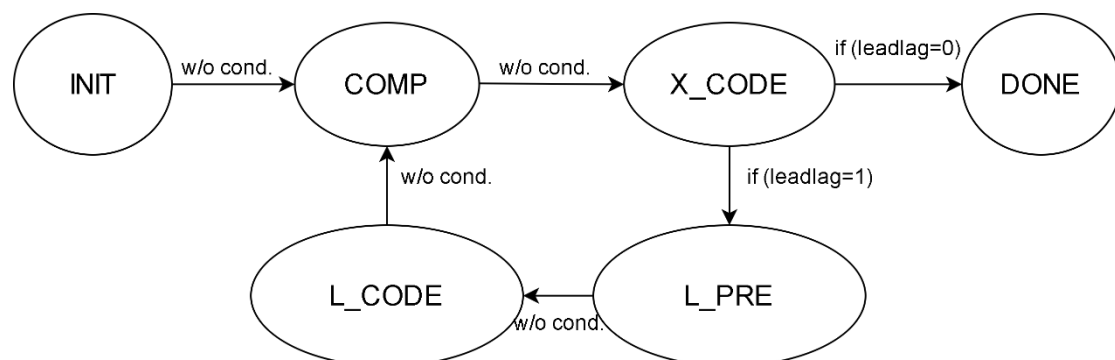(5) Controller (FSM)

這次電路的起始狀態會在 $\lambda[7:0]=8'b0000_0001$ 也就是 $x[2:0]=3'b000$ 的情況，目的是為了讓 TDL 的 delay 先設定到最小，再慢慢(一次+1)尋找 lead/lag 訊號由 1 變 0 的時候，即為目標的 control code，得到 clk_hp 接近是 clk_in 的半周期延遲訊號，並在此時讓 locked=1。以此為中心思想，又因為考慮到輸入時脈訊號為 1GHz，不算低頻的訊號，為避免後續可能有 setup time violation，因此先想辦法讓每個 state 做的事越少越好，所以將 control code 的決定分成了兩個步驟，並且還加入了一個中間 state (下圖中的 L_PRE)，目的是對即將轉變的通道做預先開啟的動作，以避免 unknown 的狀態發生，在上次作業中有較詳細解釋過理由。以下即是作為 controller 的 FSM 架構：



INIT state: DCC reset 後會到這個 state，主要負責設定電路內的初始值。

COMP state: 拉起 enable PD 的訊號，並等待 lead/lag 訊號穩定確定下來，接著在下一個 state 讀取。


X_CODE state: 依據 lead/lag 訊號，決定 $x[2:0]$ ，並停下 PD。

L_PRE state: 在更新 $\lambda[7:0]$ 之前，先預先打開通道為未知節點做充放電，避免 unknown signal 的出現。


L_CODE state: 將 $x[2:0]$ 轉換成的 one-hot code 更新 $\lambda[7:0]$ 。

DONE state: 表示電路已經準備好完成 dcc 之 clock 訊號。

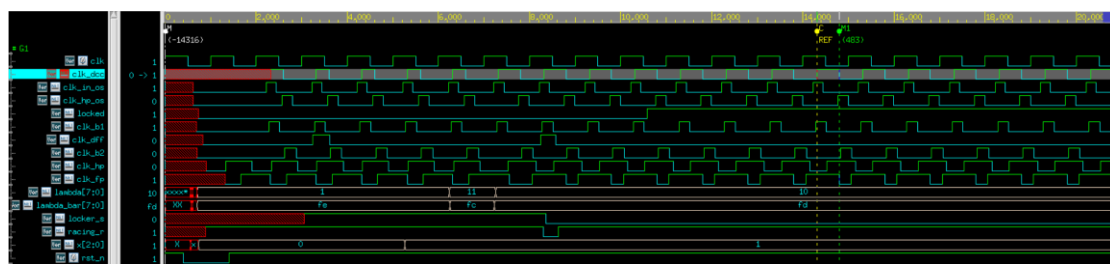在驗證電路功能時發現 input clock 的 duty cycle 為 50% 時，還是功能正常的電路，如下圖：



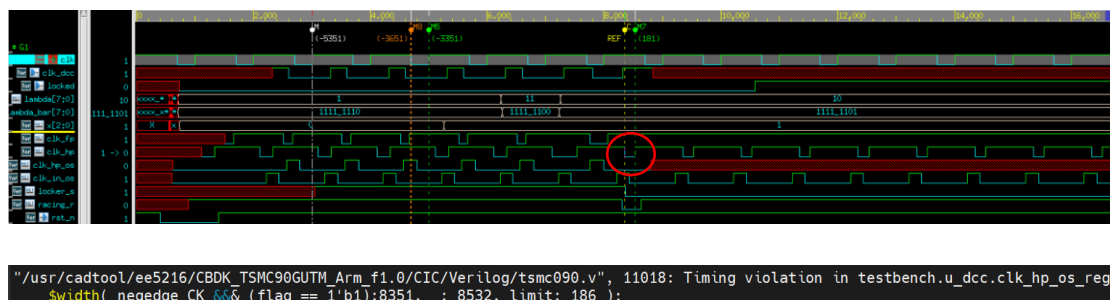到了 input clock 的 duty cycle 為 70% 時，卻發生 timing violation，波型圖與 error message 如下圖所示：



可以發現是因為 clk_fp 為 0 的時間太短了，儘管已經選用 CLKBUFF 作為 buffer，但還是因為經過許多 buffer 和 tri-state buufer 後 skew 得越來越嚴重，為解決此問題我選擇減少 buffer 數量，並同時調小 buffer 的尺寸，以獲得差不多的 delay time 但較少的 skew，最終規格是如上 TDL 架構時提過的數量及尺寸。

TDL netlist:

```
1 module delay_buffer_chain ( out, in );
2   input in;
3   output out;
4   wire n1,n2,n3;
5   CLKBUX1 U0 ( .A(in), .Y(n1) );
6   CLKBUX1 U1 ( .A(n1), .Y(n2) );
7   CLKBUX1 U2 ( .A(n2), .Y(n3) );
8
9   CLKBUX1 U4 ( .A(n3), .Y(out) );
10
11 endmodule
12
13 module delay_buffer ( out, in );
14   input in;
15   output out;
16   wire n1;
17   CLKBUX1 U0 ( .A(in), .Y(n1) );
18   CLKBUX1 U4 ( .A(n1), .Y(out) );
19
20 endmodule
21
22
23
24 module tdl (clk_in, lambda, lambda_bar, clk_out);
25   input [7:0] lambda;
26   input [7:0] lambda_bar;
27   input clk_in;
28   output clk_out;
29   wire clk_1, clk_2, clk_3, clk_4, clk_5, clk_6, clk_7, clk_8,
30         clk_2_2, clk_3_2, clk_4_2, clk_5_2, clk_6_2, clk_7_2, clk_8_2, clk_out;
31
32
33   delay_buffer_chain bcl ( .out(clk_1), .in(clk_in) );
34   delay_buffer bc2 ( .out(clk_2), .in(clk_1) );
35   delay_buffer bc3 ( .out(clk_3), .in(clk_2) );
36   delay_buffer bc4 ( .out(clk_4), .in(clk_3) );
37
38   delay_buffer bc5 ( .out(clk_5), .in(clk_4) );
39   delay_buffer bc6 ( .out(clk_6), .in(clk_5) );
40   delay_buffer bc7 ( .out(clk_7), .in(clk_6) );
41   delay_buffer bc8 ( .out(clk_8), .in(clk_7) );
42
43   TBUX4 buf_1 ( .A(clk_1), .Y(clk_out), .OE(lambda[0]));
44   TBUX4 buf_2 ( .A(clk_2), .Y(clk_2_2), .OE(lambda[1]));
45   TBUX4 buf_2_2 ( .A(clk_2_2), .Y(clk_out), .OE(lambda_bar[0]));
46   TBUX4 buf_3 ( .A(clk_3), .Y(clk_3_2), .OE(lambda[2]));
47   TBUX4 buf_3_2 ( .A(clk_3_2), .Y(clk_2_2), .OE(lambda_bar[1]));
48   TBUX4 buf_4 ( .A(clk_4), .Y(clk_4_2), .OE(lambda[3]));
49   TBUX4 buf_4_2 ( .A(clk_4_2), .Y(clk_3_2), .OE(lambda_bar[2]));
50   TBUX4 buf_5 ( .A(clk_5), .Y(clk_5_2), .OE(lambda[4]));
51   TBUX4 buf_5_2 ( .A(clk_5_2), .Y(clk_4_2), .OE(lambda_bar[3]));
52   TBUX4 buf_6 ( .A(clk_6), .Y(clk_6_2), .OE(lambda[5]));
53   TBUX4 buf_6_2 ( .A(clk_6_2), .Y(clk_5_2), .OE(lambda_bar[4]));
54   TBUX4 buf_7 ( .A(clk_7), .Y(clk_7_2), .OE(lambda[6]));
55   TBUX4 buf_7_2 ( .A(clk_7_2), .Y(clk_6_2), .OE(lambda_bar[5]));
56   TBUX4 buf_8 ( .A(clk_8), .Y(clk_8_2), .OE(lambda[7]));
57   TBUX4 buf_8_2 ( .A(clk_8_2), .Y(clk_7_2), .OE(lambda_bar[6]));
58
59
60 endmodule
```

DCC RTL code:

```
1 `include "tdl.v"
2
3 module dcc (
4   output clk_dcc,
5   output locked,
6   input clk,
7   input rst_n
8 );
9
10 //////////////////////////////////////////////////
11 //DECLARATION
12 //////////////////////////////////////////////////
13 //TDL signals
14 wire clk_fp, clk_hp;
15 reg [7:0] lambda;
16 reg [7:0] lambda_bar;
17 reg [7:0] lambda_next, lambda_prenext;
18 wire [7:0] lambda_bar_next, lambda_bar_prenext;
19 reg [2:0] x;
20
21 //PD signals
22 wire direction;
23 reg clk_dff;
24 reg clk_fp_dff;
25 wire rst_pd;
26 wire rst_pd_flag;
27 wire pd_en;
28 wire pd_dummy;
29 wire racing_s, racing_r;
30 wire locker_s, locker_r;
31
32 //one shot circuit
33 reg clk_in_os, clk_hp_os;
34 wire rst_os1, rst_os2;
35 wire clk_b1, clk_b2;
36
37 //output SR latch
38 wire q, q_bar;
39
40 //state
41 localparam ST_INIT = 3'b000;
42 localparam ST_X_CODE = 3'b001;
43 localparam ST_L_PRE = 3'b010;
44 localparam ST_L_CODE = 3'b011;
45 localparam ST_COMP = 3'b100;
46
47 localparam ST_DONE = 3'b110;
48
49 reg [2:0] state;
50 reg [2:0] state_nx;
51
52 //FSM
53 //setting next state
54 always@(posedge clk or negedge rst_n)begin
55   if(~rst_n) state <= ST_INIT;
56   else state <= state_nx;
57 end
58
59 //decision of next state
60 always@(*)begin
61   state_nx = state;
62   case(state)
63     ST_INIT : state_nx = ST_COMP;
64     ST_X_CODE :
65       begin
66         if(direction) state_nx = ST_L_PRE;
67         else state_nx = ST_DONE;
68       end
69     ST_L_PRE : state_nx = ST_L_CODE;
70     ST_L_CODE : state_nx = ST_COMP;
```

```

73 ST_COMP : state_nx = ST_X_CODE;
74
75 ST_DONE : state_nx = state;
76 default : state_nx = state;
77 endcase
78 end
79
80 //output controlled by FSM
81 assign locked = (state == ST_DONE);
82 assign pd_en = (state==ST_COMP); //for PD
83
84 //Searching process
85 //Searching process
86 //Searching process
87 //lambda code decision - x value
88 always@(posedge clk or negedge rst_n) begin
89     if(~rst_n) x <= 3'b000;
90     else begin
91         case(state)
92             ST_INIT : x <= 3'b000;
93             ST_X_CODE :
94                 begin
95                     if(direction) x <= x + 1;
96                     else x <= x; //or x-1
97                 end
98             ST_L_PRE, ST_L_CODE, ST_COMP, ST_DONE : x <= x;
99             default : x <= x;
100         endcase
101     end
102 end
103
104 //lambda comb. logic
105 always@(*) begin
106     case(x)
107         3'b000: lambda_next = 8'b00000001;

```

```

145     else begin
146         case(state)
147             ST_INIT : begin
148                 lambda <= 8'b00000001;
149                 lambda_bar <= 8'b11111110;
150             end
151             ST_X_CODE, ST_COMP, ST_DONE : begin
152                 lambda <= lambda;
153                 lambda_bar <= lambda_bar;
154             end
155             ST_L_PRE : begin
156                 lambda <= lambda_prenext;
157                 lambda_bar <= lambda_bar_prenext;
158             end
159             ST_L_CODE : begin
160                 lambda <= lambda_next;
161                 lambda_bar <= lambda_bar_next;
162             end
163             default : begin
164                 lambda <= lambda;
165                 lambda_bar <= lambda_bar;
166             end
167         endcase
168     end
169 end
170
171 //Phase Detector
172 //PD
173 //PD
174 //PD
175 //PD
176 always @(posedge clk_fp or negedge rst_pd) begin
177     if(~rst_pd) clk_fp_dff <= 0;
178     else clk_fp_dff <= 1;
179 end
180

```

```

109     3'b001: lambda_next = 8'b00000010;
110     3'b010: lambda_next = 8'b00000100;
111     3'b011: lambda_next = 8'b00001000;
112     3'b100: lambda_next = 8'b00010000;
113     3'b101: lambda_next = 8'b00100000;
114     3'b110: lambda_next = 8'b01000000;
115     3'b111: lambda_next = 8'b10000000;
116     default: lambda_next = 8'b00000010;
117 endcase
118 end
119
120 assign lambda_bar_next = ~ lambda_next;
121
122 always@(*) begin
123     case(x)
124         3'b000: lambda_prenext = 8'b00000001;
125         3'b001: lambda_prenext = 8'b00000011;
126         3'b010: lambda_prenext = 8'b00000110;
127         3'b011: lambda_prenext = 8'b00001100;
128         3'b100: lambda_prenext = 8'b00011000;
129         3'b101: lambda_prenext = 8'b00110000;
130         3'b110: lambda_prenext = 8'b01100000;
131         3'b111: lambda_prenext = 8'b11000000;
132         default: lambda_prenext = 8'b00000011;
133     endcase
134 end
135
136 assign lambda_bar_prenext = ~ lambda_prenext;
137
138 //lambda update
139 always@(posedge clk or negedge rst_n) begin
140     if(~rst_n) begin
141         lambda <= 8'b00000001;
142         lambda_bar <= 8'b11111110;
143     end
144 end

```

```

181 always @(posedge clk or negedge rst_pd) begin
182     if(~rst_pd) clk_dff <= 0;
183     else clk_dff <= 1;
184 end
185
186 assign rst_pd_flag = ~ (clk_fp_dff & clk_dff);
187 assign pd_dummy = ~(clk_dff & clk_fp_dff);
188 assign rst_pd = pd_en & rst_pd_flag;
189
190 //SR latch as racing circuit
191 assign racing_s = ~ (racing_r & clk_fp_dff);
192 assign racing_r = ~ (racing_s & clk_dff);
193
194 //SR latch as signal locker
195 assign locker_s = ~ (locker_r & racing_s);
196 assign locker_r = ~ (locker_s & racing_r);
197
198 //direction = 1 if clk_fp is faster, which means we need to tune a
199 assign direction = locker_s;
200
201 //One Shot Circuit
202 //One Shot Circuit
203 //One Shot Circuit
204 //one-shot-based osc. 1
205 always @(posedge clk or negedge rst_os1 or negedge rst_n) begin
206     if(~rst_n) clk_in_os <= 0;
207     else if(~rst_os1) clk_in_os <= 0;
208     else clk_in_os <= 1;
209 end
210
211 delay_buffer ub_1 (.out(clk_b1), .in (clk_in_os));
212 assign rst_os1 = ~clk_b1;
213
214 //one-shot-based osc. 2
215 always @(posedge clk_hp or negedge rst_os2 or negedge rst_n) begin
216     if(~rst_n) clk_hp_os <= 0;

```


```

217     else if(~rst_os2) clk_hp_os <= 0;
218     else clk_hp_os <= 1;
219 end
220
221 delay_buffer ub_2 (.out(clk_b2), .in (clk_hp_os));
222 assign rst_os2 = ~clk_b2;
223
224
225 //////////////////////////////////////////////////
226 //Tunable Delay Line
227 //////////////////////////////////////////////////
228 //instantiate
229 tdl tdl_1 (
230     .clk_out (clk_hp),
231     .clk_in  (clk),
232     .lambda  (lambda),
233     .lambda_bar (lambda_bar)
234 );
235
236 tdl tdl_2 (
237     .clk_out (clk_fp),
238     .clk_in  (clk_hp),
239     .lambda  (lambda),
240     .lambda_bar (lambda_bar)
241 );
242
243 //////////////////////////////////////////////////
244 //Output Stage SR Latch
245 //////////////////////////////////////////////////
246 assign q_bar = ~ (clk_in_os | q);
247 assign q = ~ (clk_hp_os | q_bar);
248
249 assign clk_dcc = q;
250
251
252 endmodule


```

Time resolution estimation:

 
在模擬時可以看到當 lambda code 從 8'b0000_0001 到 8'b0000_0010，兩條 TDL 的 delay time 總和在兩個情況下相差 1141-679=462ps，波形如下圖：



對單條 TDL 做 gate-level simulation，得到波形如下圖：

 

局部放大圖：

 

可以發現當 lambda code 從 8'b0000_0001 到 8'b0000_0010，單條 TDL 的 delay time 在兩個情況下相差 579-348=231ps (兩條就會是 462ps)，與實際應用在 DCC 電路中的結果是相符的。之後的 lambda code 每增加 1 格，TDL 的 delay time 就會增加 230ps，篇幅關係就不貼上局部的波形圖。

因此結論是單個 TDL 的 time resolution 大約在 230 到 231ps 之間，若看兩個 TDL 則 time resolution 大約在 460 到 462ps 之間。

- (c) (15%) Try to use Design Compiler to **synthesize your design into standard-cell netlists**. Report the gate count of your netlist.

合成時使用的.tcl 檔：

```
1 set ref_cycle 1
2 set DESIGN_TOP dcc
3 /*----- 1.Read files -----*/
4 /*----- 1.Read files -----*/
5 /*----- 1.Read files -----*/
6 analyze -format verilog {../1.RTL_simulation/dcc.v}
7 elaborate $DESIGN_TOP
8 set_operating_conditions -min_library fast -min fast \
9 -max_library slow -max slow
10 /*----- 2. Set design constraints -----*/
11 /*----- 2. Set design constraints -----*/
12 /*----- 2. Set design constraints -----*/
13 create_clock -name CLK -period $ref_cycle [get_ports clk]
14 set_dont_touch_network [get_ports clk]
15 set_fix_hold [get_clocks CLK]
16 # input drive / output load
17 set_drive 1 [all_inputs]
18 set_load [load_of slow/CLKBUF20/A] [all_outputs]
19 /*----- 2.5 保護 TDL (不要讓 DC 動裡面的 gate) -----*/
20 /*----- 2.5 保護 TDL (不要讓 DC 動裡面的 gate) -----*/
21 /*----- 2.5 保護 TDL (不要讓 DC 動裡面的 gate) -----*/
22 set_dont_touch [get_designs tdl]
23 set_dont_touch [get_cells -hierarchical tdl_1]
24 set_dont_touch [get_cells -hierarchical tdl_2]
25 /*----- 3.Check and Link Design -----*/
26 /*----- 3.Check and Link Design -----*/
27 /*----- 3.Check and Link Design -----*/
28 link
29 check_design
30 uniquify
31 set_fix_multiple_port_nets -all -buffer_constants
32 /*----- 4.Compile -----*/
33 /*----- 4.Compile -----*/
34 /*----- 4.Compile -----*/
35 # Setting DRC Constraint
36 set_max_fanout 20.0 $DESIGN_TOP
37 # Area Constraint
38 set_max_area 0
39 # before synthesis settings
40 set_case_analysis_with_logic_constants true
41 set_fix_multiple_port_nets -all -buffer_constants
42 set_clock_gating_style -max_fanout 10
43 compile -map_effort medium
44 # remove dummy ports
45 remove_unconnected_ports [get_cells -hierarchical *]
46 remove_unconnected_ports [get_cells -hierarchical *] -blast_buses
47 check_design
48 # rename / bus style
49 set_bus_inference_style {%s[%d]}
50 set_bus_naming_style {%s[%d]}
51 set_hdlout_internal_busses true
52 set_verilogout_show_unconnected_pins true
53 /*----- 5.Write out files -----*/
54 /*----- 5.Write out files -----*/
55 /*----- 5.Write out files -----*/
56 report_area > ./dcc_syn.report
57 report_timing -path full -delay max >> ./dcc_syn.report
58 report_power >> ./dcc_syn.report
59 write -format verilog -hierarchy -output ./dcc_syn.v
60 write_sdf -version 2.1 -context verilog -load_delay cell ./dcc_syn.sdf
61 write_sdc ../3.Post_layout_Simulation/APR/design_data/dcc_syn.sdc
62 exit
```

合成出的 netlist 就不附上了，實在有點冗長。合成後的面積如下：

Number of ports:	76
Number of nets:	249
Number of cells:	210
Number of combinational cells:	133
Number of sequential cells:	56
Number of macros/black boxes:	0
Number of buf/inv:	57
Number of references:	47
Combinational area:	497.448013
Buf/Inv area:	162.993604
Noncombinational area:	643.507208
Macro/Black Box area:	0.000000
Net Interconnect area:	undefined (No wire load specified)
Total cell area:	1140.955220

使用 total cell area $1140.95522\mu m^2$ ，可以除以 2-input NAND gate 的面積 $2.82\mu m^2$ ，換算成 gate count 約為 404.6。

- (d) (15%) Verify the correctness of your design by running gate-level Verilog simulation using as accurate delay model as possible. Show the waveforms of *clk_in* and *clk_dcc*. Try the following input duty cycle samples for *clk_in* – {30%, 70%}. **Report the final duty cycle for each input samples.**


Testbench 的部分很簡單，只有給予 *clk* 和 *rst_n*，並等待 *locked* 後結束模擬：

```

1 `timescale 100ps / 10ps
2 module testbench;
3
4     localparam period = 10;
5     localparam delay = 4;
6
7     reg      clk;
8     wire     clk_dcc;
9     reg      rst_n;
10    wire     locked;
11
12    dcc u_dcc (
13        .clk_dcc(clk_dcc),
14        .locked(locked),
15        .clk(clk),
16        .rst_n(rst_n)
17    );
18
19    initial begin
20        $sdf_annotate("./dcc_syn.sdf", u_dcc);
21        $fsdbDumpfile("../4.Simulation_Result/dcc_syn.fsdb");
22        $fsdbDumpvars;
23    end
24
25
26    initial begin
27        clk = 1;
28        forever begin
29            #(3) clk = 0;
30            #(7) clk = 1;
31        end
32    end
33
34    initial begin
35        rst_n = 1;
36        #(delay) rst_n = 0;
37        #(period) rst_n = 1;
38        wait(locked);
39
40        #(period * 6) $finish;
41    end
42
43    // Automatically finish
44    initial begin
45        #30000;
46        $finish;
47    end
48
49 endmodule


```

輸入時脈訊號 **duty cycle 為 30%** 的模擬結果：

 

可以看到 *clk_dcc* 在 DCC 鎖定後的 duty cycle = $\frac{523 \text{ ps}}{1000 \text{ ps}} = 52.3\%$ 。

輸入時脈訊號 **duty cycle 為 70%** 的模擬結果：

 

可以看到 *clk_dcc* 在 DCC 鎖定後的 duty cycle = $\frac{523 \text{ ps}}{1000 \text{ ps}} = 52.3\%$ 。